




USER ACCESS
NAME ATTACHED TO HIS ID
ACCESS APPROVED
DNA CONFIRMS THE GENETIC INFORMATION
ALLOWING ALL MODERN LIVING
1 BILLION YEARS SCAN DONE
ACCESS DENIED
RETURN ACCESS SCAN
ACCESS APPROVED, WELCOME
ENTER YOUR PASS CODE
XXXXXXXXXX

ELEC1100 - Tutorial 3

Pulse and PWM Control


Introduction to Lab#03

Preview – what's at physical lab

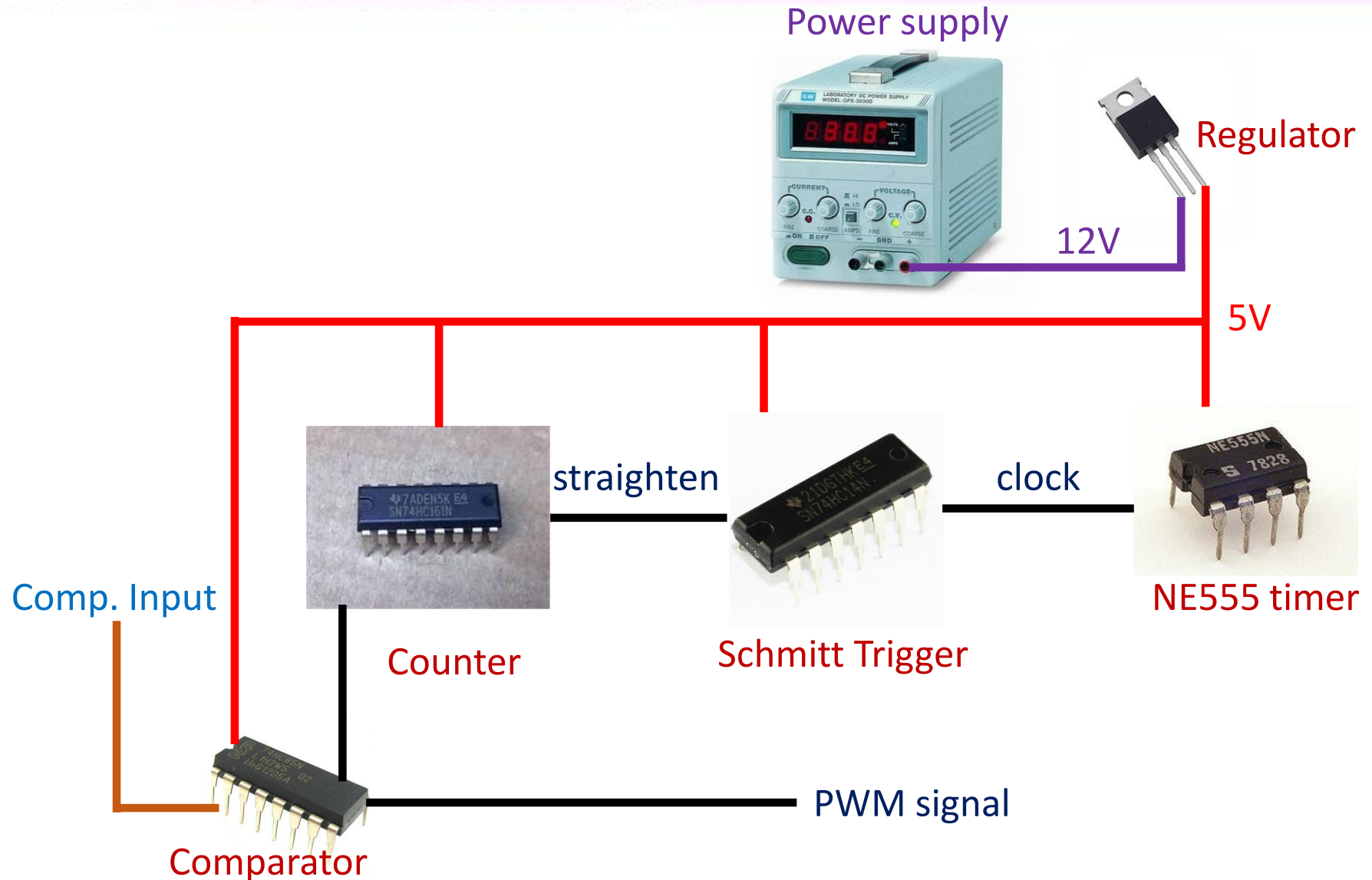



Pulse Signal

❖ A rectangular pulse looks like this.

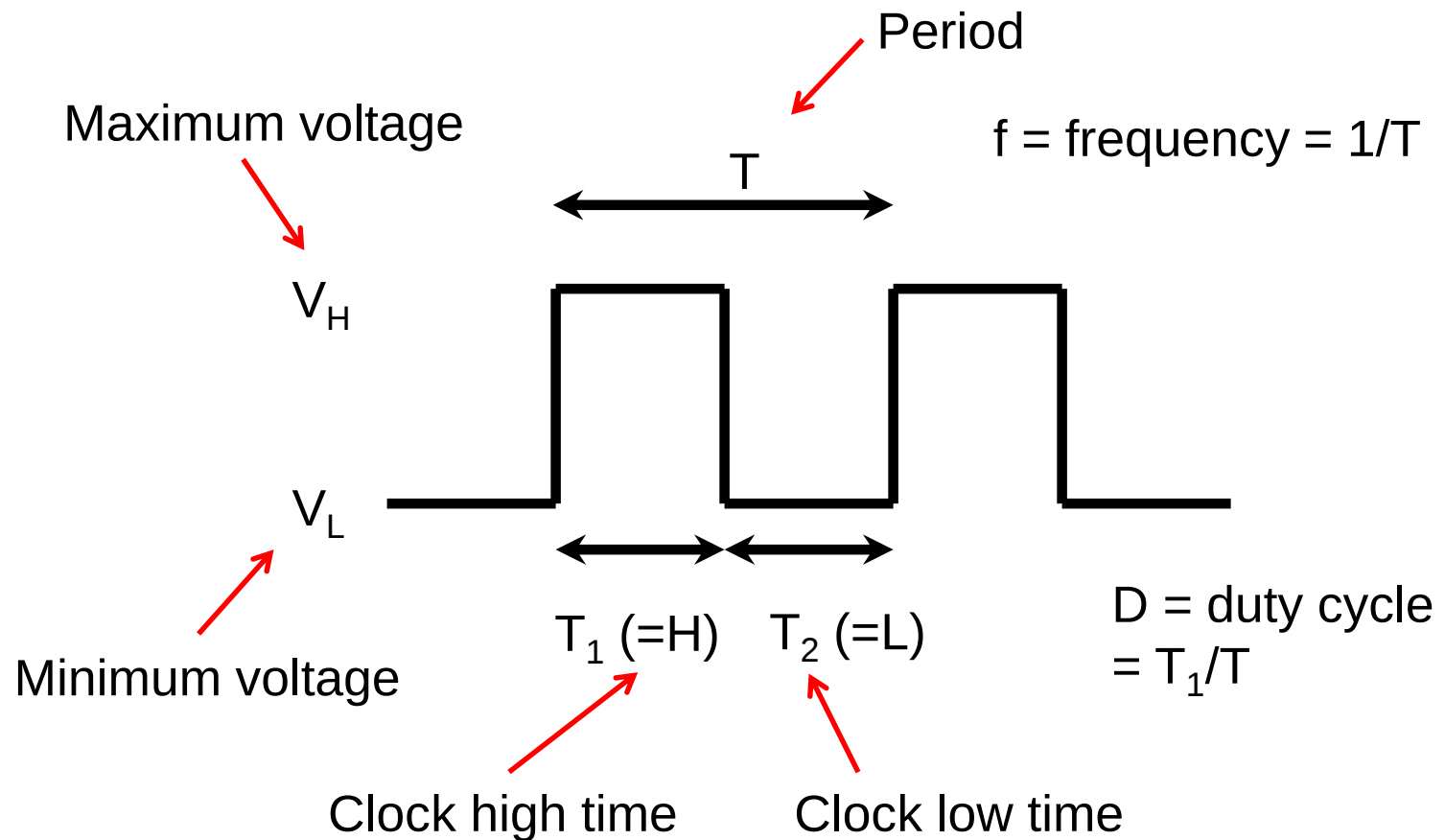

NE555 Timer Circuit

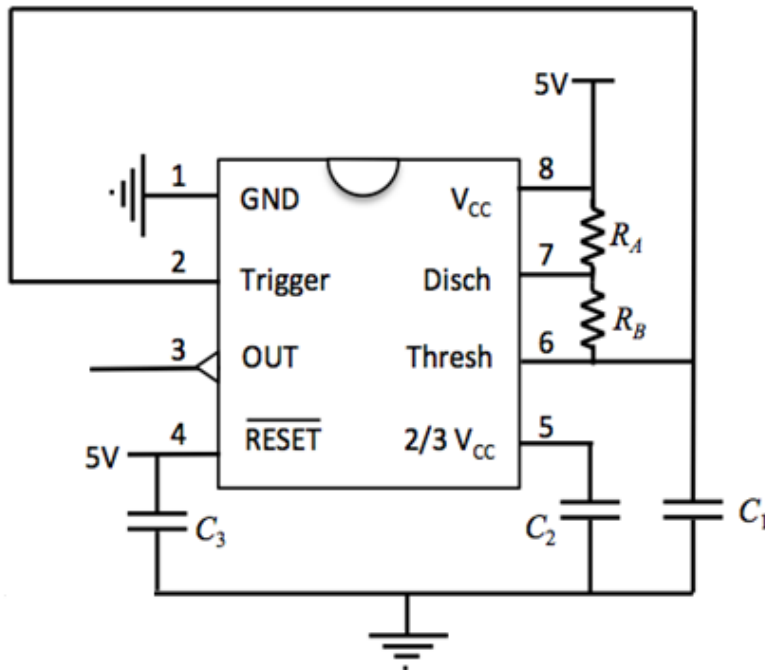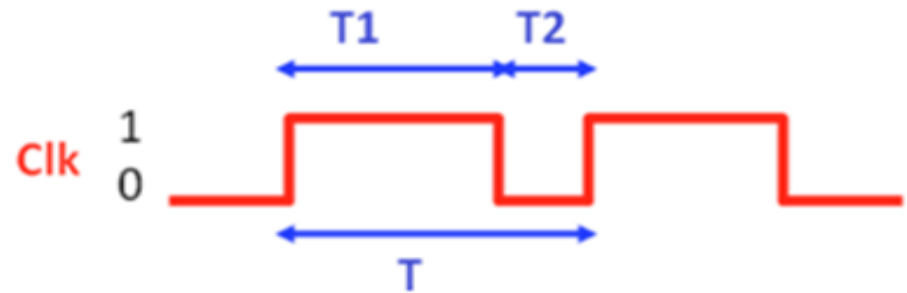❖ This is a NE555 timer. Equations given.



$$T1 = 0.7 (R_A + R_B) C_1$$

$$T2 = 0.7 (R_B) C_1$$

$$T = 0.7 (R_A + 2R_B) C_1$$

Observation:

Duty Cycle $\geq$ 50%


NE555 Timer Circuit

Lab#03: Simulation 2

$$R_A = 30k\Omega \quad R_B = 10k\Omega$$

$$C_1 = C_2 = C_3 = 0.1\mu F$$

Frequency = ? Duty cycle = ?

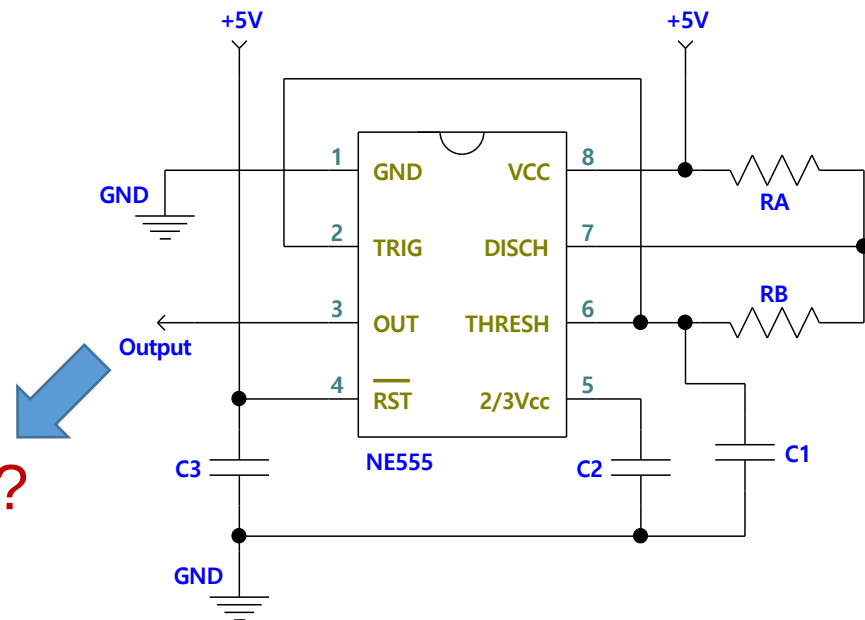


$$\text{Frequency} = \frac{1}{T} = \frac{1}{0.7(R_A + 2R_B)C_1} \approx 286\text{Hz}$$

$$\text{Duty cycle} = \frac{R_A + R_B}{R_A + 2R_B} = 80\%$$

In Tinkercad

Lab#03: Simulation 2

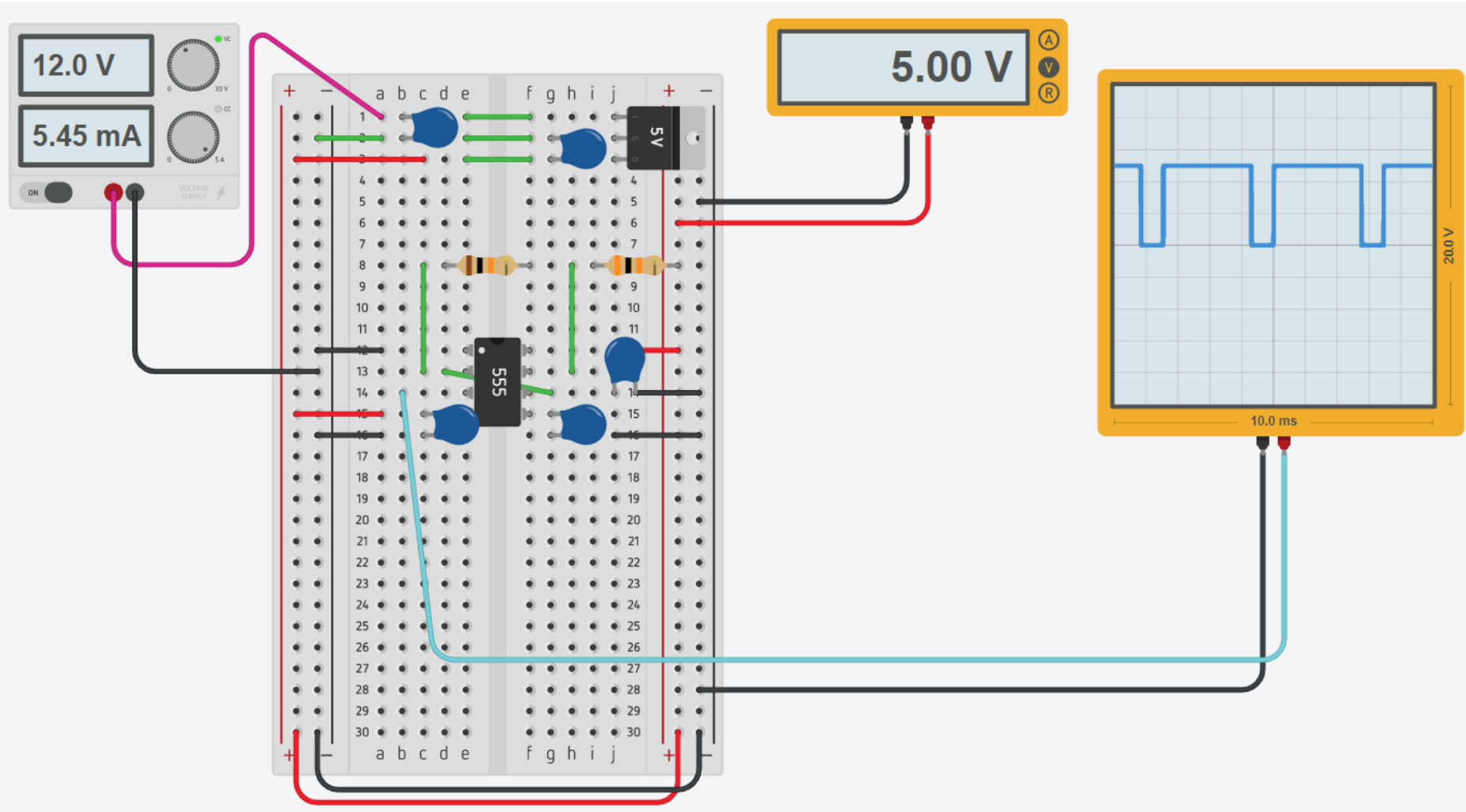


Schmitt Trigger 74HC14

Practical output of timer:



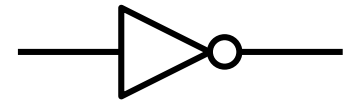
Solution: Schmitt Trigger. Straighten up the pulse




✓ There are 6 Schmitt Triggers and you only need to use one
14 pins, 6 pairs

✓ The V_{CC} (positive supply) and GND has to be connected to power for proper function

1, 2, 7, 14

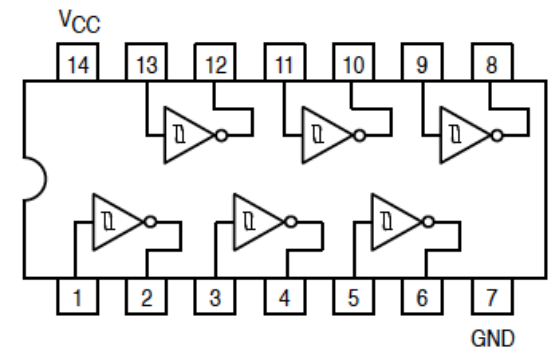

+

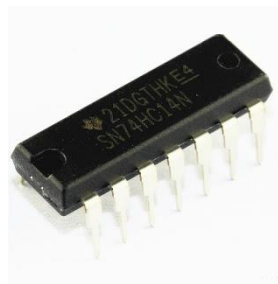

=




****The output is inverted**



NE555 + 74HC14


Lab#03: Simulation 3

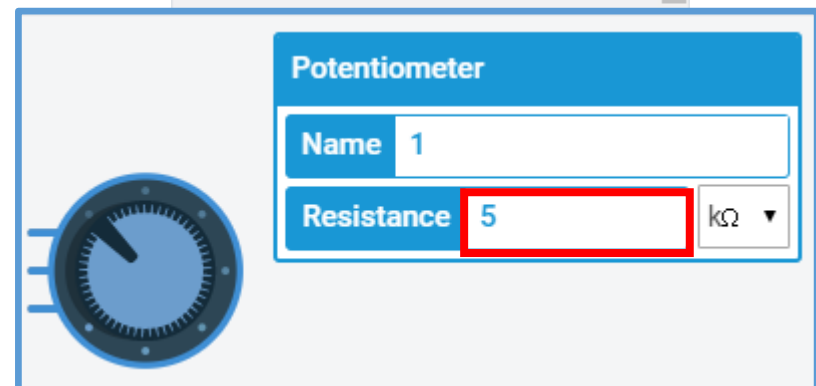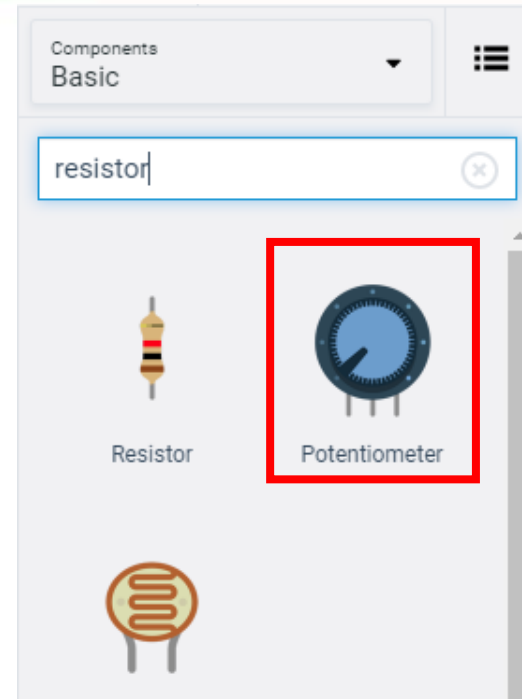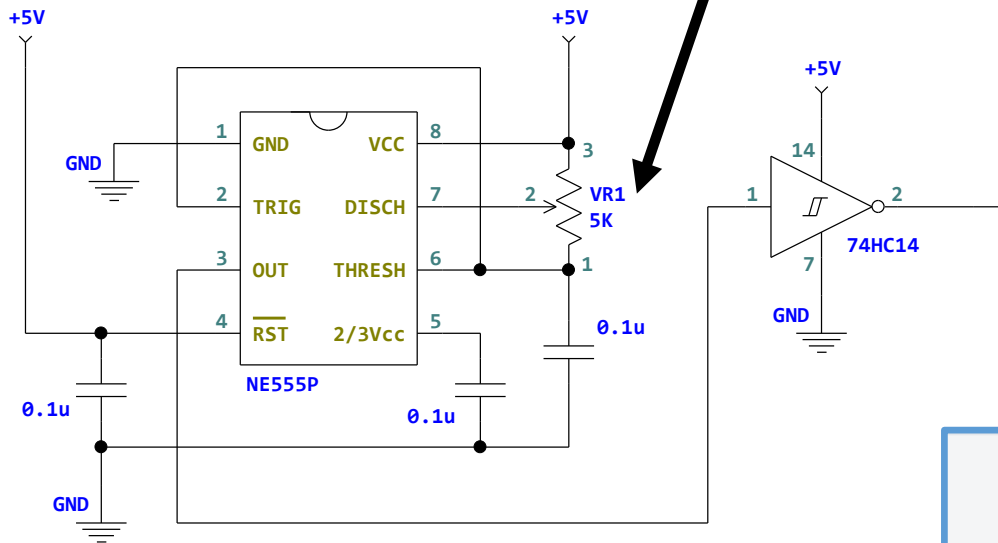Use a variable resistor to
replace R_A and R_B



In Tinkercad

Lab#03: Simulation 3

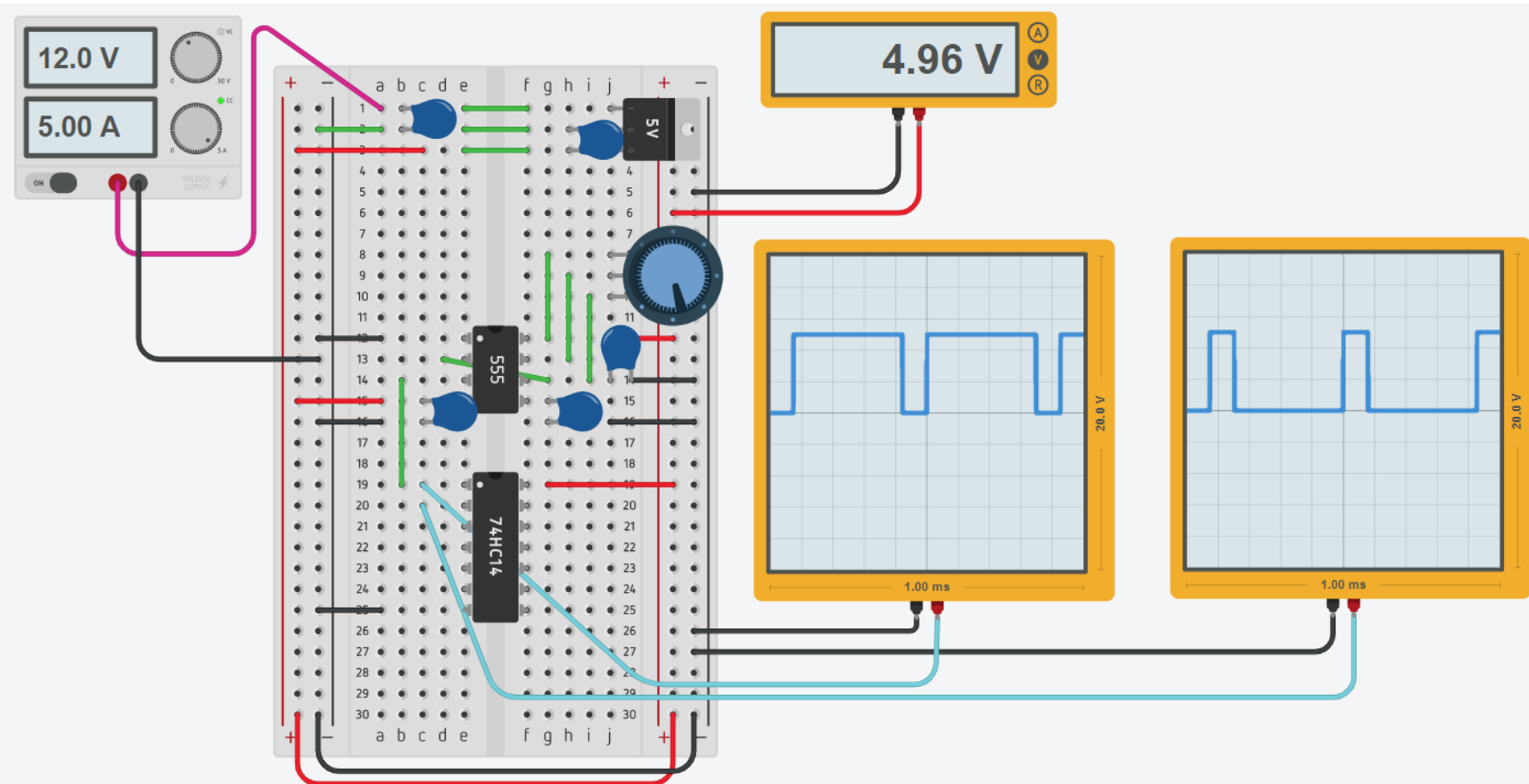

❖ Let's say you use a pulse to drive a motor

- By changing resistances, we can form **pulses** with variable duty cycles => adjust **motor** speed
- But we can't change the hardware while the **motor** is moving!
- We need a way to change the duty cycle without modifying the hardware
 - The change will be determined by the circuit itself


HOW?

74HC161 & 74HC85

❖ 74HC161 4-bit Binary Counter



- It does this:

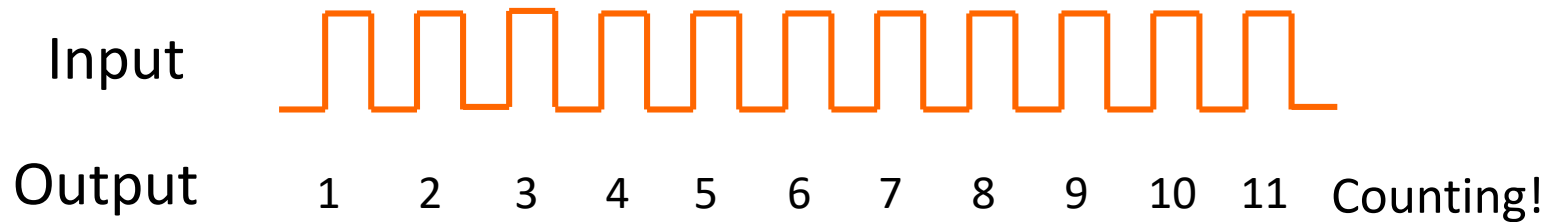


Note: Output are in binary, i.e. 9 → 1001


❖ 74HC85 4-bit Comparator

- Compares two inputs and output:
- "<", "=", ">"

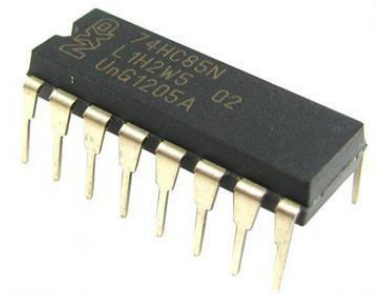By combining these devices, we can change the duty cycle



Schematic

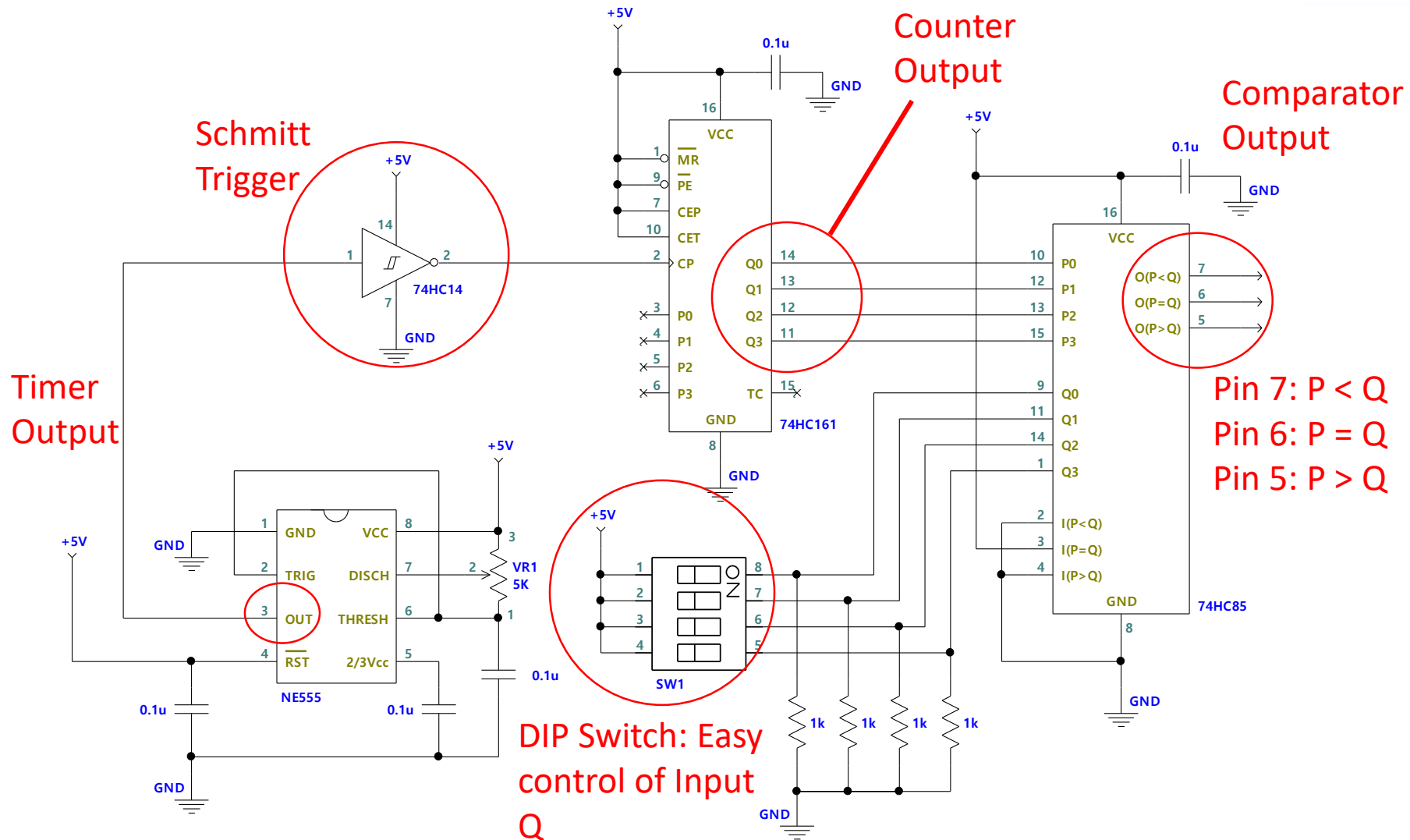

PWM Signal

❖ Use the counter to count, then use the comparator to determine the duty cycle

Q: Frequency = ?

Clock



74HC161 0 1 2 3 4 5 6 7 8 9 10 11 12 13 14 15 0 1

Compare to 12 12 12 12 12 12 12 12 12 12 12 12 12 12 12 12 12 12

74HC85

"<"



Compare to 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7 7

74HC85

"<"



❖ Suppose we use PWM to control motor

- Pin 7 (P < Q) of comparator is 100Hz
- Duty cycle = 0.75

Q1: Manual input Q = ? $0.75 \times 16 = 12 \rightarrow 1100$

Q2: Period of NE555 timer? $1 / (100 \times 16) = 625\mu s$

Q3: Given $C_1 = 0.1\mu F$, what are the theoretical resistance values of the two parts of $5k\Omega$ variable resistor R_A and R_B ?

$$T = 1/1600 = 0.7(R_A + 2R_B) C_1 \rightarrow R_A + 2R_B = 8929\Omega \quad (1)$$

$$\text{(Given the variable resistance } 5k\Omega) \quad R_A + R_B = 5000\Omega \quad (2)$$

$$\rightarrow R_A = 1071\Omega, R_B = 3929\Omega$$

- In Lab#03, we will construct NE555 Timer and 74HC14 Schmitt Trigger circuits (online version).
- For 74HC161 counter and 74HC85 comparator circuits, we only study on how to use them to generate the PWM signal at theory level.
- We will use Arduino board to generate the PWM signal in your project.